

# WEEK 2

## INTERNSHIP UNDER DR GS JAVED SIR

INTERN NAME - AFZAL MALIK

COLLEGE/UNIVERSITY – ZAKIR HUSAIN COLLEGE OF ENGG. & TECH.  
ALIGARH MUSLIM UNIVERSITY

COURSE- BACHELOR OF TECHNOLOGY (ELECTRONICS ENGG.)

YEAR – SECOND

## WEEK 2 INTERNSHIP PLAN

- Differential Pair simulation
- Current Mirror simulation
- Delay Cell simulation
- Comparator simulation

SOFTWARE USED : LT Spice

# SIMPLE CURRENT MIRROR

DESIGN AND SIMULATION USING LT SPICE  
MODEL FILE : 180n

## SPECIFICATIONS


$I_{ref}=50\mu A$  is used for  $I_d(M2) = 500\mu A$

# SCHEMATIC

## SIMPLE CURRENT MIRROR (IDEAL CURRENT SOURCE AS REFERENCE)

SPECIFICATION:  $I_{ref}=50\mu A$

.include tsmc180.txt  
.op

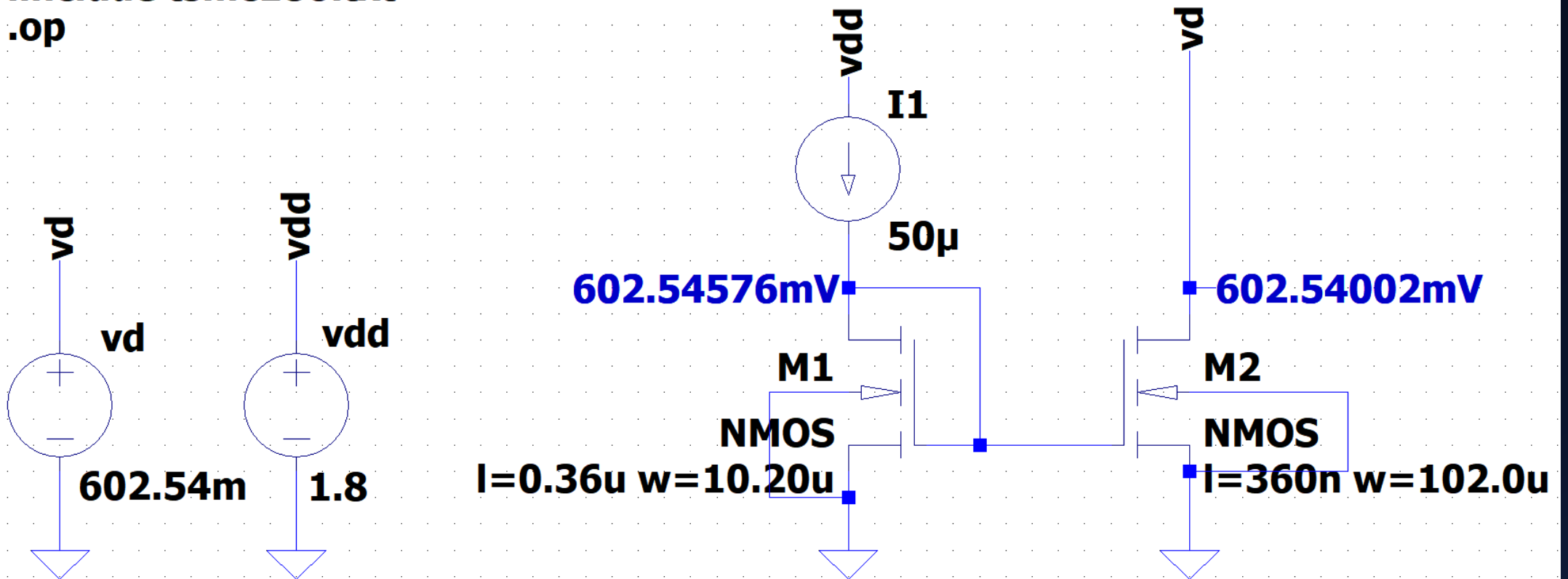

## SPICE ERROR LOG

### Semiconductor Device Operating Points:

--- BSIM3 MOSFETS ---

Name:	m2	m1
Model:	nmos	nmos
Id:	5.16e-04	5.00e-05
Vgs:	6.03e-01	6.03e-01
Vds:	6.00e-01	6.03e-01
Vbs:	0.00e+00	0.00e+00
Vth:	4.64e-01	4.66e-01
Vdsat:	1.09e-01	1.07e-01
Gm:	8.09e-03	7.93e-04
Gds:	7.55e-05	7.37e-06
Gmb	2.13e-03	2.09e-04
Cbd:	0.00e+00	0.00e+00
Cbs:	0.00e+00	0.00e+00

Iref= Id(M1) = 50uA    AND    Id(M2) = 516uA

# SIMPLE CURRENT MIRROR

DESIGN AND SIMULATION USING LT SPICE  
MODEL FILE : 180n


## SPECIFICATIONS

$I_{ref}=50\mu A$  is used for  $I_d(M2) = 500\mu A$

Note: Ideal Current Source is replaced by Diode connected PMOS

# SCHEMATIC

.include tsmc180.txt  
.op

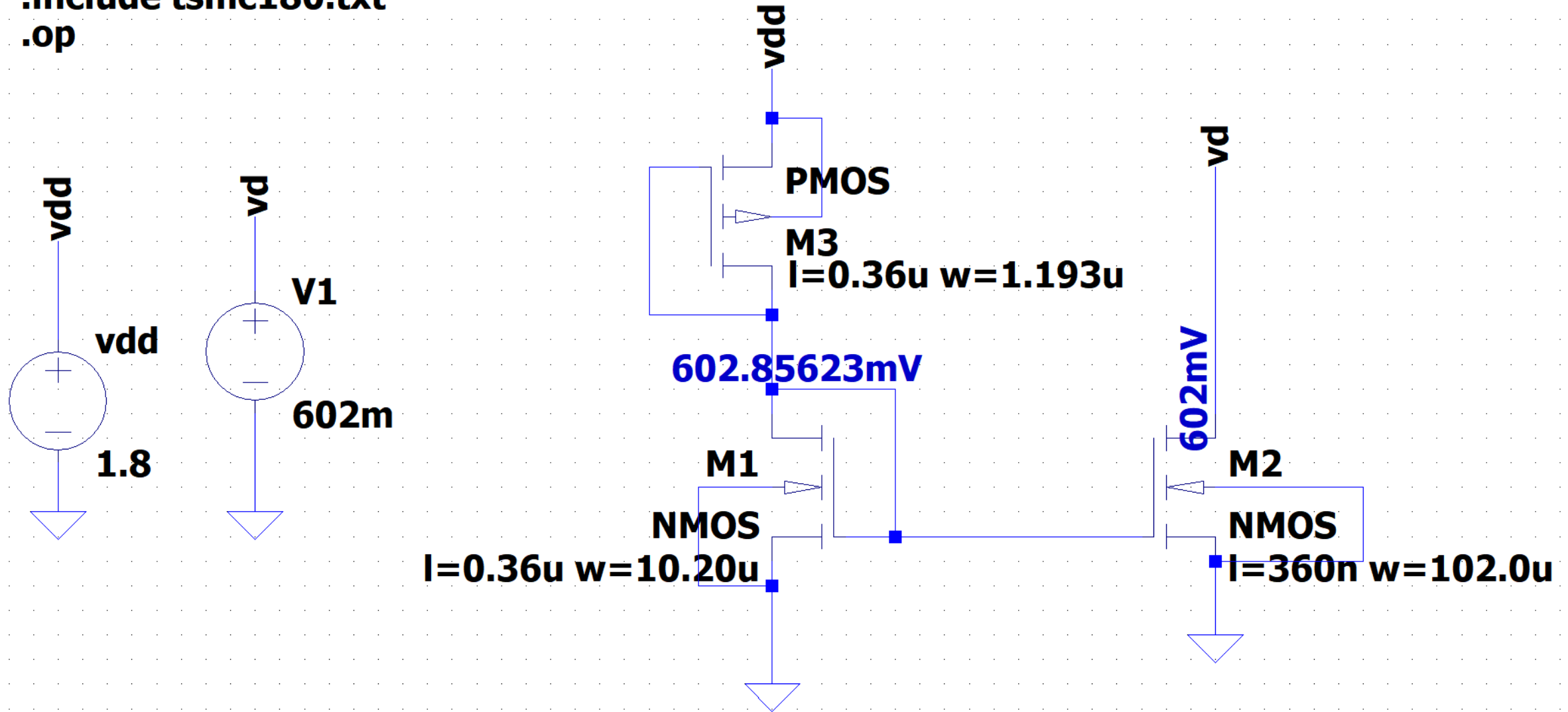

## SPICE ERROR LOG

Semiconductor Device Operating Points:

--- BSIM3 MOSFETS ---

Name:	m3	m2	m1
Model:	pmos	nmos	nmos
Id:	-5.02e-05	5.19e-04	5.02e-05
Vgs:	-1.20e+00	6.03e-01	6.03e-01
Vds:	-1.20e+00	6.02e-01	6.03e-01
Vbs:	0.00e+00	0.00e+00	0.00e+00
Vth:	-4.67e-01	4.64e-01	4.66e-01
Vdsat:	-5.50e-01	1.09e-01	1.07e-01
Gm:	1.18e-04	8.12e-03	7.96e-04
Gds:	3.59e-06	7.57e-05	7.40e-06
Gmb	3.88e-05	2.14e-03	2.10e-04
Cgd	0.00e+00	0.00e+00	0.00e+00

Iref= Id(M1) = 50uA    AND    Id(M2) = 519uA



# CASCODE CURRENT MIRROR

DESIGN AND SIMULATION USING LT SPICE  
MODEL FILE : 180n



## SPECIFICATIONS

$I_{ref}=50\mu A$  is used for  $I_d(M2) = 500\mu A$

# SCHEMATIC

## CASCODE CURRENT MIRROR SPECIFICATION: $I_{ref}=50\mu A$

.include tsmc180.txt  
.op

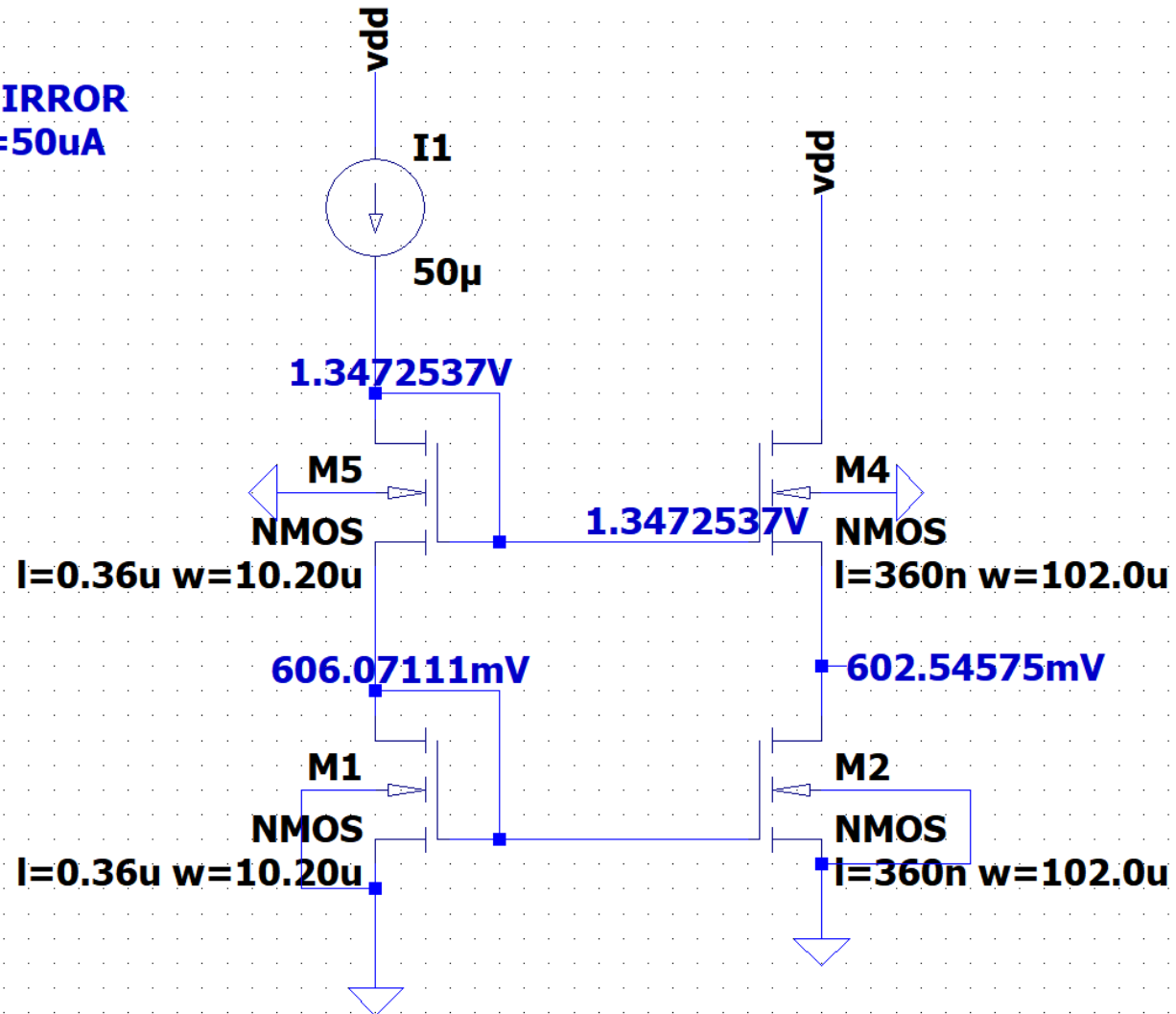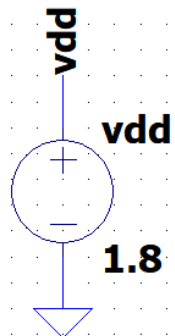

## SPICE ERROR LOG

Semiconductor Device Operating Points:

--- BSIM3 MOSFETS ---

Name:	m5	m4	m2	m1
Model:	nmos	nmos	nmos	nmos
Id:	5.00e-05	5.16e-04	5.16e-04	5.00e-05
Vgs:	7.45e-01	7.41e-01	6.03e-01	6.03e-01
Vds:	7.45e-01	1.19e+00	6.06e-01	6.03e-01
Vbs:	-6.03e-01	-6.06e-01	0.00e+00	0.00e+00
Vth:	6.21e-01	6.19e-01	4.64e-01	4.66e-01
Vdsat:	1.12e-01	1.11e-01	1.09e-01	1.07e-01
Gm:	8.10e-04	8.31e-03	8.09e-03	7.93e-04
Gds:	7.39e-06	6.94e-05	7.53e-05	7.37e-06
Gmb	1.76e-04	1.79e-03	2.13e-03	2.09e-04
Cbd:	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cgsov:	7.85e-15	7.85e-14	7.85e-14	7.85e-15

$I_{ref} = I_d(M1) = 50\mu A$     AND     $I_d(M2) = 516\mu A$

# DIFFERENTIAL PAIR

DESIGN AND SIMULATION USING LT SPICE  
MODEL FILE : 180n

## SPECIFICATIONS


GBW = 1GHz

Gain = 10 at 100 MHz frequency
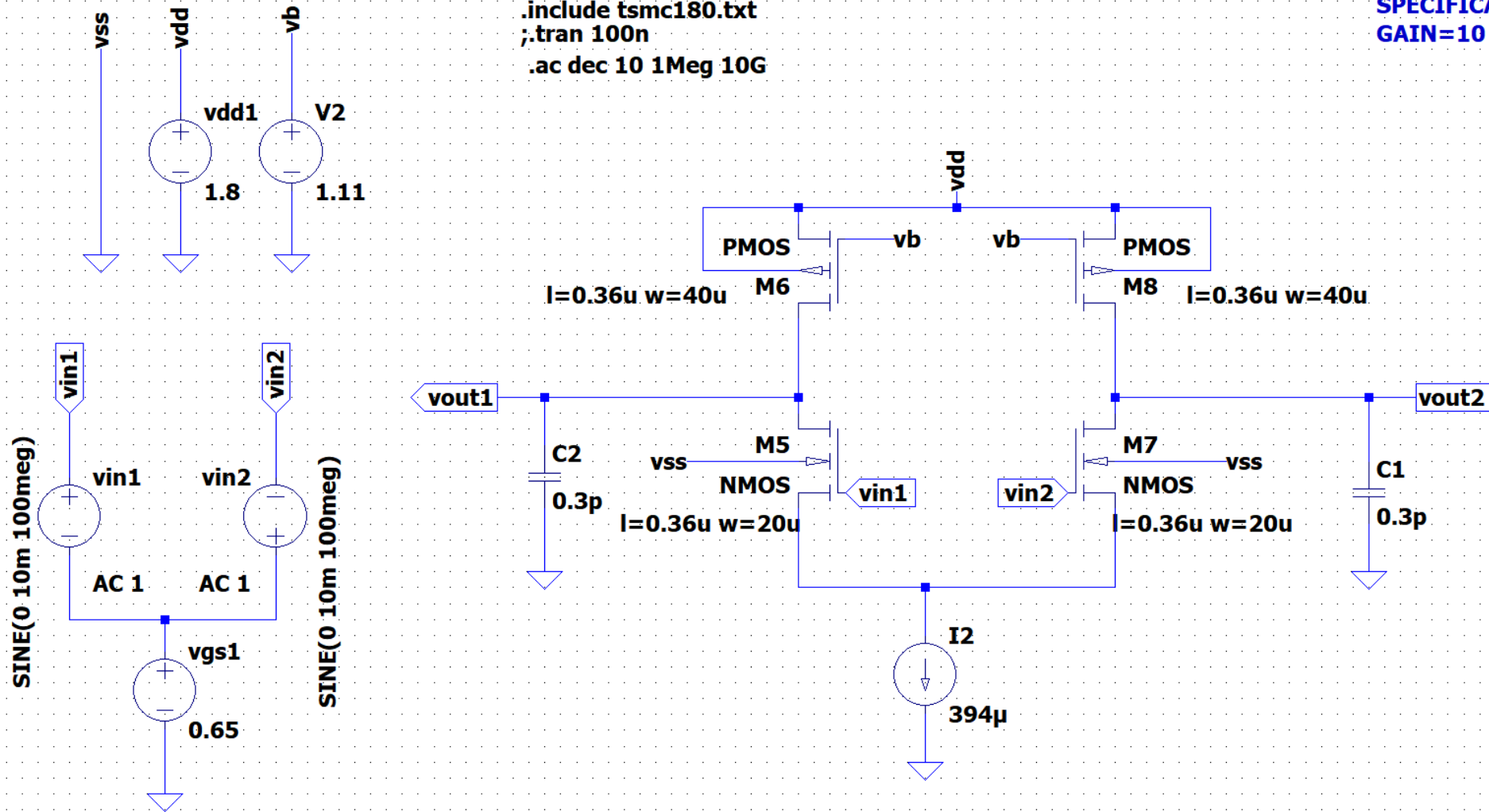
# SCHEMATIC

```
.op
;tf V(vout1,vout2) (vin1,vin2)
.include tsmc180.txt
;.tran 100n
.ac dec 10 1Meg 10G
```

**DIFFERENTIAL PAIR**  
**SPECIFICATION: GBW=1GHz**  
**GAIN=10 AT 100MHz**



## SPICE ERROR LOG

### Semiconductor Device Operating Points:


--- BSIM3 MOSFETS ---

Name:	m8	m6	m7	m5
Model:	pmos	pmos	nmos	nmos
Id:	-1.97e-04	-1.97e-04	1.97e-04	1.97e-04
Vgs:	-6.90e-01	-6.90e-01	6.50e-01	6.50e-01
Vds:	-9.82e-01	-9.82e-01	8.18e-01	8.18e-01
Vbs:	0.00e+00	0.00e+00	-8.44e-07	-8.44e-07
Vth:	-4.73e-01	-4.73e-01	4.65e-01	4.65e-01
Vdsat:	-1.94e-01	-1.94e-01	1.41e-01	1.41e-01
Gm:	1.68e-03	1.68e-03	2.39e-03	2.39e-03
Gds:	1.69e-05	1.69e-05	2.22e-05	2.22e-05
Gmb	5.39e-04	5.39e-04	6.26e-04	6.26e-04
Cbd:	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cgsov:	2.84e-14	2.84e-14	1.54e-14	1.54e-14
Cgdov:	2.84e-14	2.84e-14	1.54e-14	1.54e-14
Cgbov:	3.11e-19	3.11e-19	3.33e-19	3.33e-19

### --- Transfer Function ---


Transfer_function:	-61.0825	transfer	
vin1#Input_impedance:	1e+020	impedance	
output_impedance_at_V(vout1,vout2):	51098.9	impedance	

# FREQUENCY RESPONSE

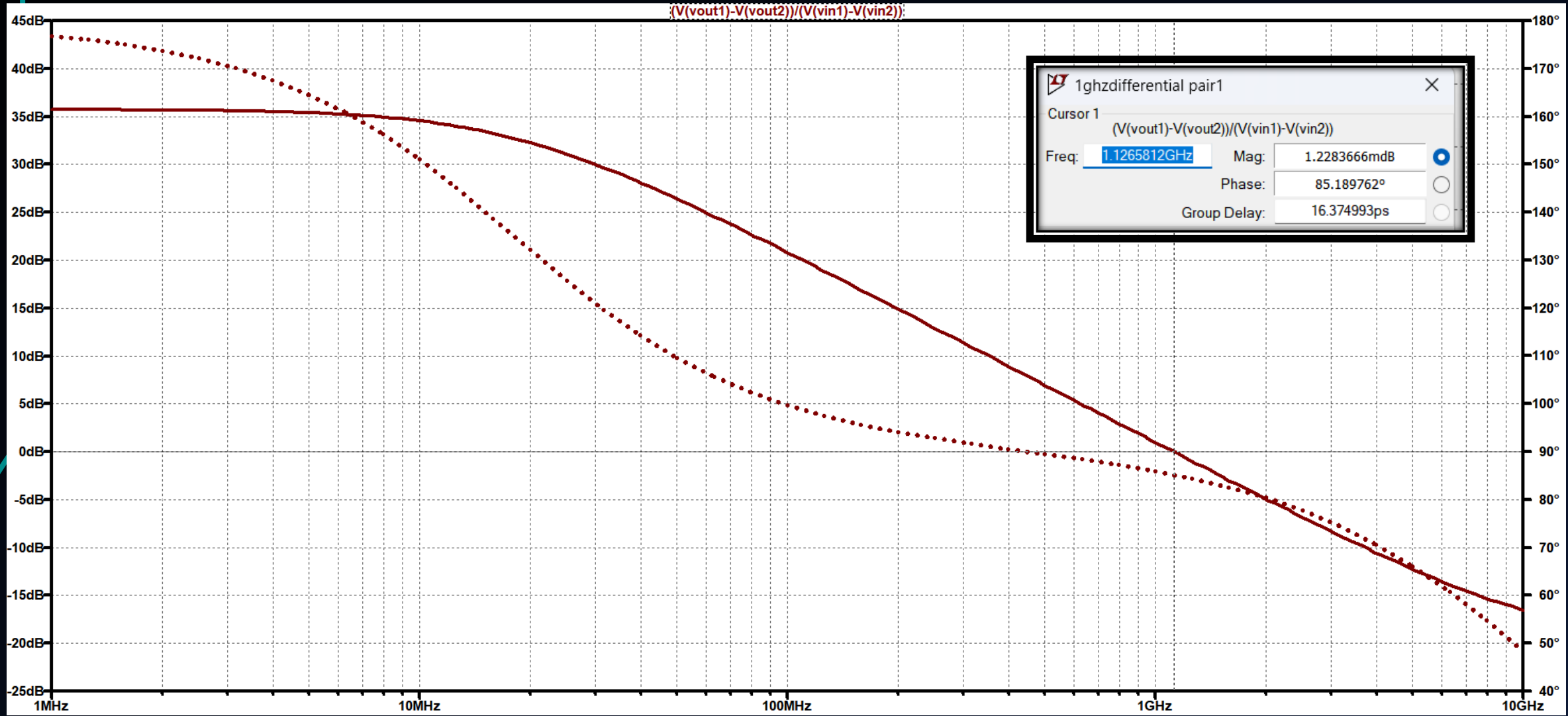

GBW=1.12GHz


# FREQUENCY RESPONSE

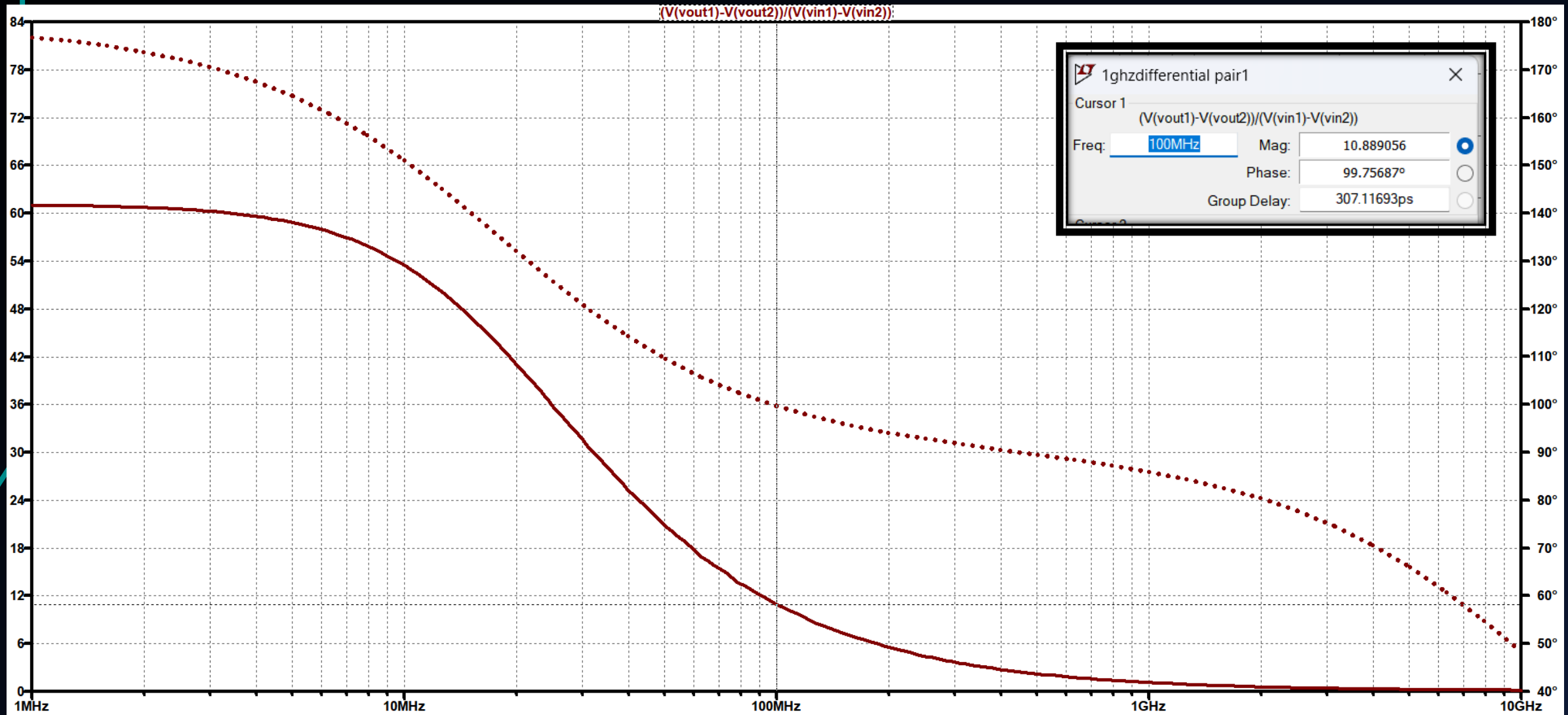

AT 100MHz Gain =10.88



# TRANSIENT ANALYSIS


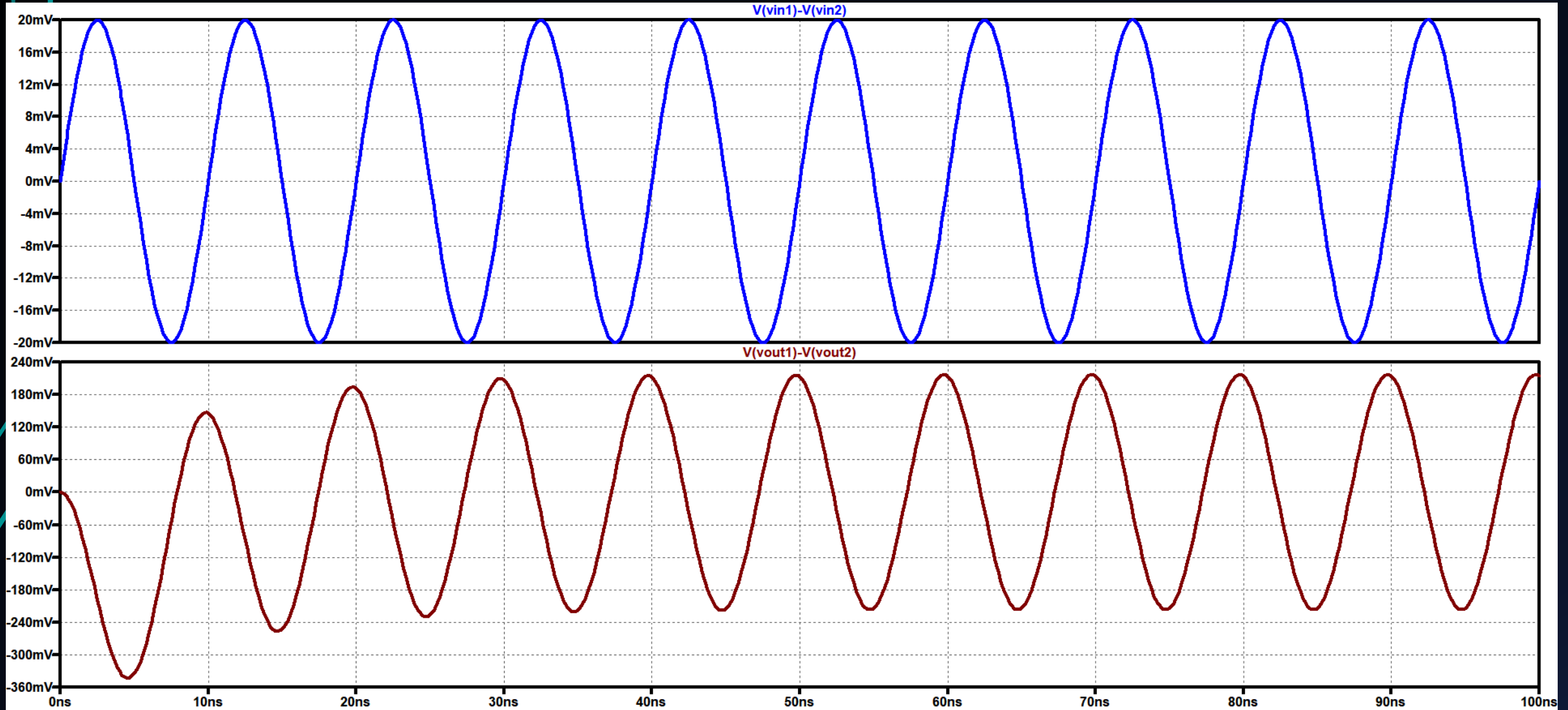


If 10mV signal is given at 100MHz then we can observe from here Gain is nearly 10
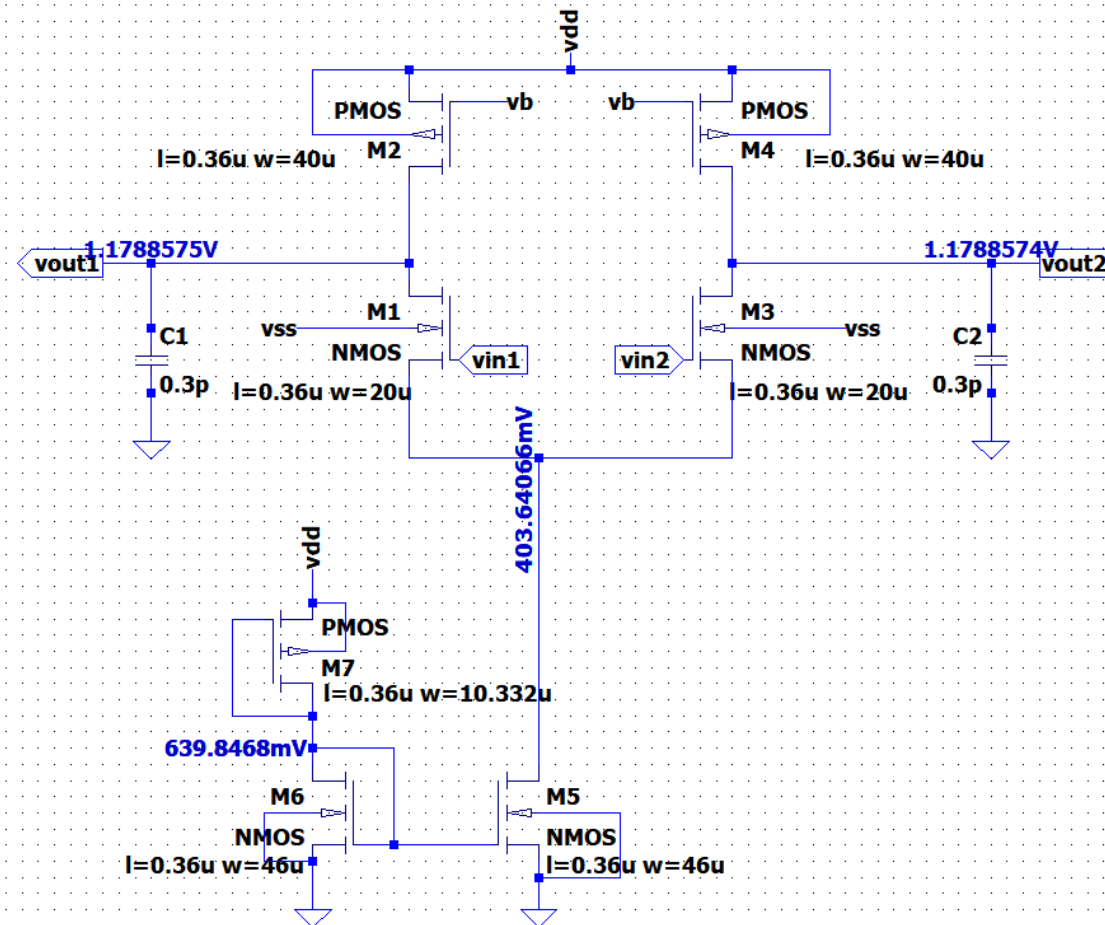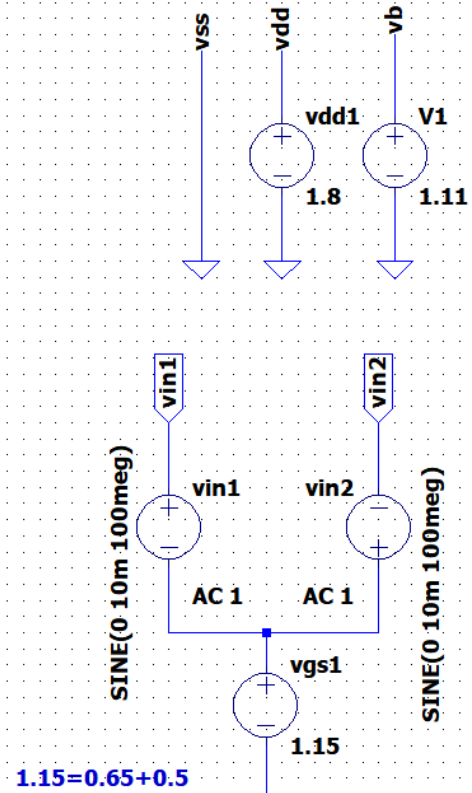
## SCHEMATIC

```
.op
;tf V(vout1,vout2) (vin1,vin2)
.include tsmc180.txt
.tran 100n
;ac dec 10 1Meg 100G
```

**DIFFERENTIAL PAIR**  
**SPECIFICATION: GBW=1GHz**  
**GAIN=10 AT 100MHz**



# SPICE ERROR LOG

## Semiconductor Device Operating Points:

--- BSIM3 MOSFETS ---


Name:	m7	m4	m2	m6	m5
Model:	pmos	pmos	pmos	nmos	nmos
Id:	-3.95e-04	-1.91e-04	-1.91e-04	3.95e-04	3.82e-04
Vgs:	-1.16e+00	-6.90e-01	-6.90e-01	6.40e-01	6.40e-01
Vds:	-1.16e+00	-6.21e-01	-6.21e-01	6.40e-01	4.04e-01
Vbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Vth:	-4.73e-01	-4.73e-01	-4.73e-01	4.64e-01	4.64e-01
Vdsat:	-5.39e-01	-1.94e-01	-1.94e-01	1.35e-01	1.35e-01
Gm:	9.73e-04	1.63e-03	1.63e-03	5.07e-03	4.94e-03
Gds:	2.79e-05	1.75e-05	1.75e-05	4.99e-05	6.26e-05
Gmb:	3.28e-04	5.21e-04	5.21e-04	1.33e-03	1.29e-03
Cbd:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cgsov:	7.35e-15	2.84e-14	2.84e-14	3.54e-14	3.54e-14
Cgdov:	7.35e-15	2.84e-14	2.84e-14	3.54e-14	3.54e-14
Cgbov:	3.11e-19	3.11e-19	3.11e-19	3.33e-19	3.33e-19
dQgdVgb:	3.74e-14	1.45e-13	1.45e-13	1.78e-13	1.79e-13
dQgdVdb:	-7.35e-15	-2.85e-14	-2.85e-14	-3.54e-14	-3.55e-14
dQgdVsb:	-2.97e-14	-1.13e-13	-1.13e-13	-1.35e-13	-1.35e-13

Name:	m3	m1
Model:	nmos	nmos
Id:	1.91e-04	1.91e-04
Vgs:	7.46e-01	7.46e-01
Vds:	7.75e-01	7.75e-01
Vbs:	-4.04e-01	-4.04e-01
Vth:	5.73e-01	5.73e-01
Vdsat:	1.45e-01	1.45e-01
Gm:	2.36e-03	2.36e-03
Gds:	2.30e-05	2.30e-05
Gmb:	5.39e-04	5.39e-04
Cbd:	0.00e+00	0.00e+00
Cbs:	0.00e+00	0.00e+00
Cgsov:	1.54e-14	1.54e-14
Cgdov:	1.54e-14	1.54e-14
Cgbov:	3.33e-19	3.33e-19

--- Transfer Function ---


Transfer_function:	-58.179	transfer
vin1#Input_impedance:	1e+020	impedance
output_impedance_at_V(vout1,vout2):	49365	impedance

# FREQUENCY RESPONSE

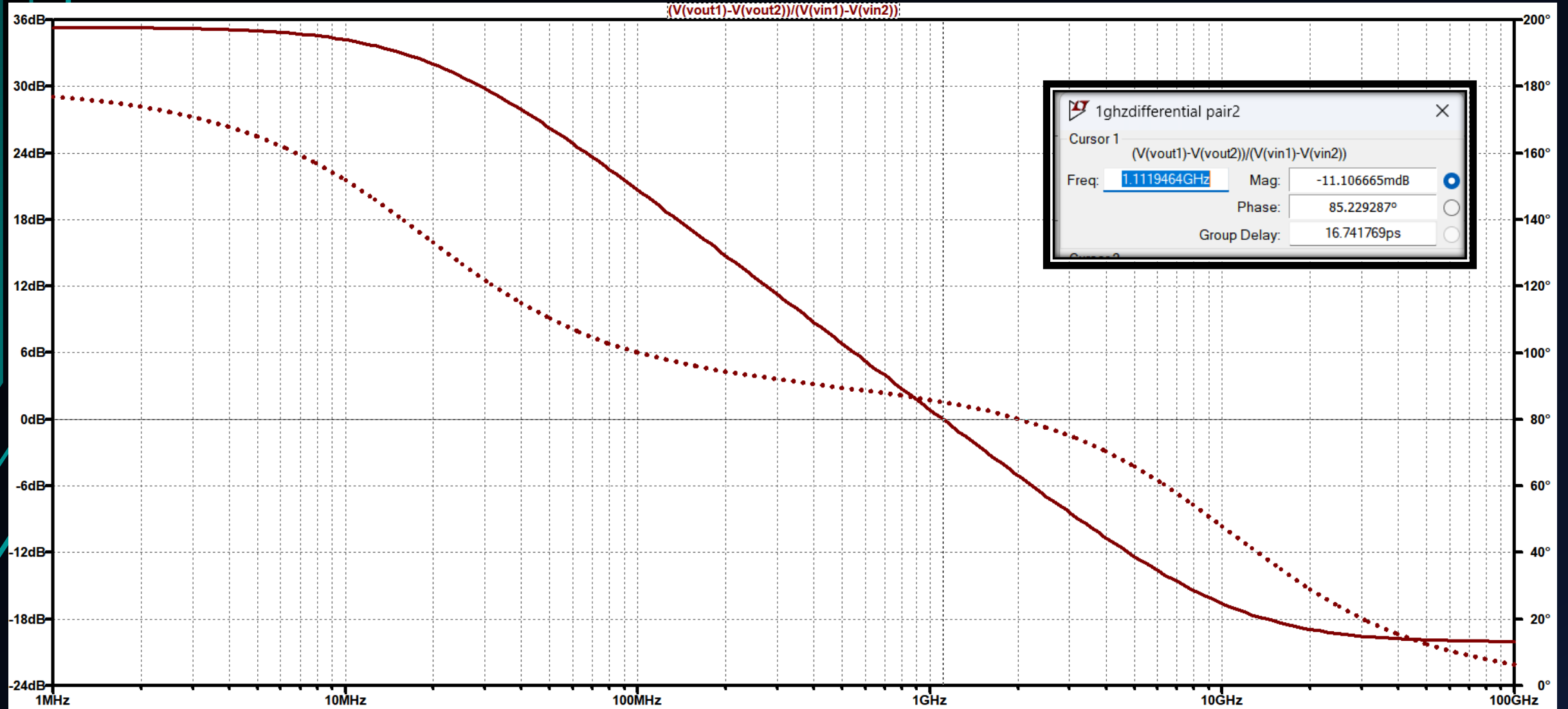


GBW=1.119GHz

# FREQUENCY RESPONSE

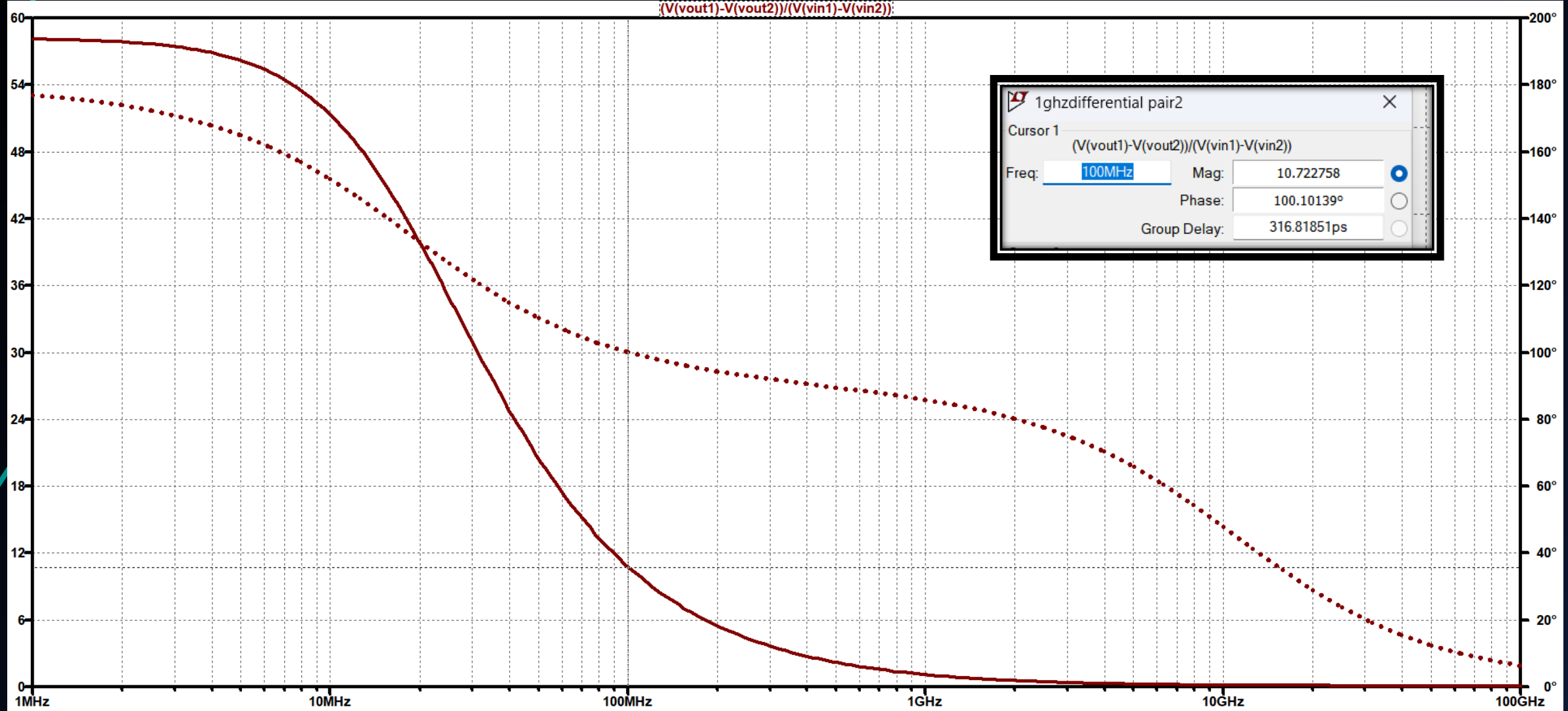

AT 100MHz Gain = 10.722

# TRANSIENT ANALYSIS

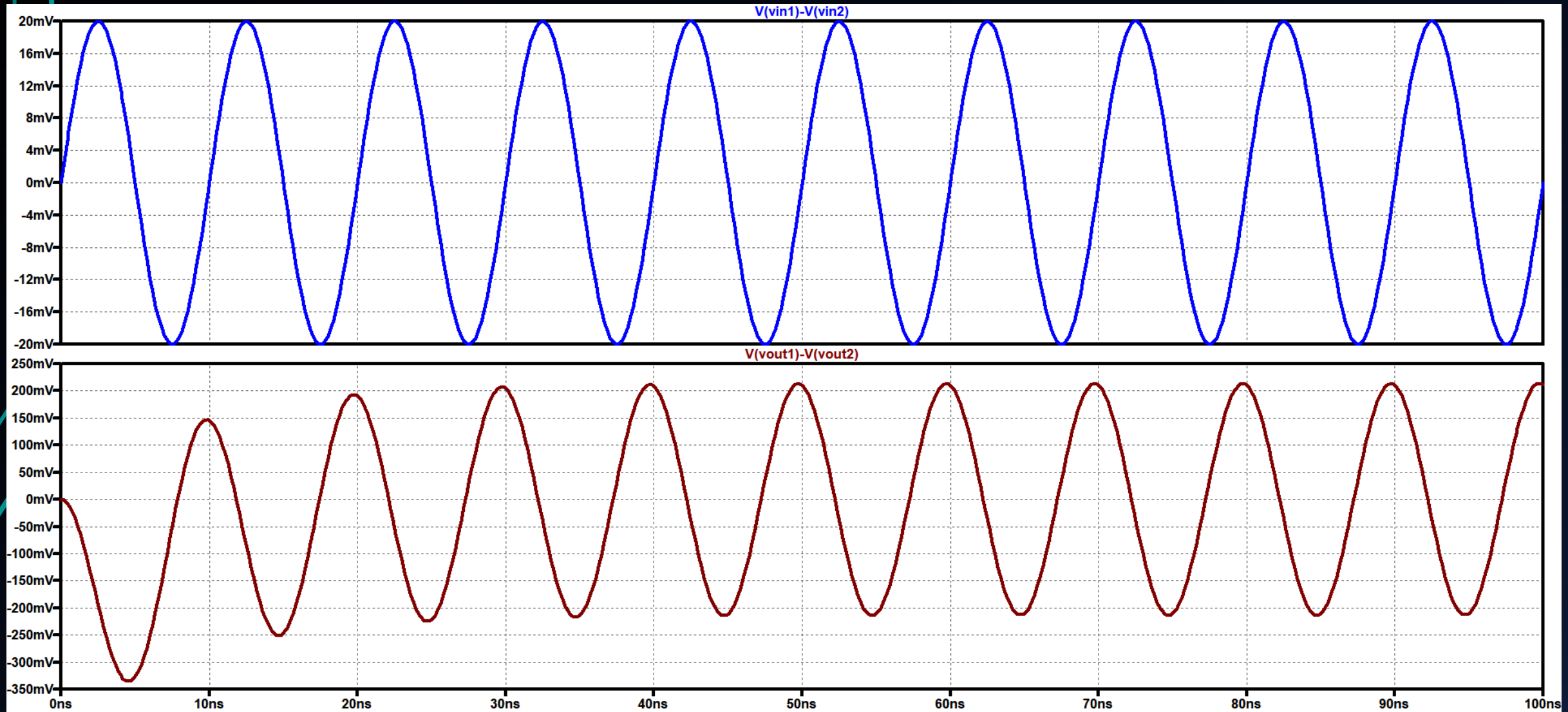

If 10mV signal is given at 100MHz then we can observe from here Gain is nearly 10



*THANK YOU*